

Heaven's Light is Our Guide

Rajshahi University of Engineering & Technology

Department of Electrical & Computer Engineering LAB REPORT

❖ Course title(Sessional) : Digital Techniques

Sessional

 ❖ Course Code
 : ECE-2112

 ❖ Date of submission
 : 22/01/2025

Submitted By :	Submitted To :
Name : Sanumong Marma	Md. Omaer Faruq Goni
Roll : 2210061	Assistant Professor
Reg no. : 1115	Department of ECE,
Series : 22	RUET
Department of ECE, RUET	

Lab no.: 02

Experiment name: Study of 4-bit adder subtractor using Verilog and DEEDS simulator Theory: In Digital Circuits, A Binary Adder-Subtractor is can do both the addition and subtraction of binary numbers in one circuit itself. The operation is performed depending on the binary value the control signal holds. It is one of the components of the ALU (Arithmetic Logic Unit). A Binary Adder is an electronic circuit that sums two binary numbers. The most basic types are half adders and full adders. A half adder takes in two one-bit numbers, producing a sum and a carry bit. Full adder has three input bits-two actual bits and an incoming carry from the preceding operation. This makes the Full Adder to add multi-bit binary numbers as the carry can propagate through a number of Full Adders in a ripple-carry adder configuration. A Binary Subtractor is used to perform the subtraction of two binary numbers. Just as in the case of addition, this also can be done using an array of logic gates. The subtraction is done by using two's complement, in which the circuit first negates the binary number to obtain its complement and then adds one to the result before imputing it into a binary adder circuit together with the original number. Both addition and subtraction are handled by this type of circuit.

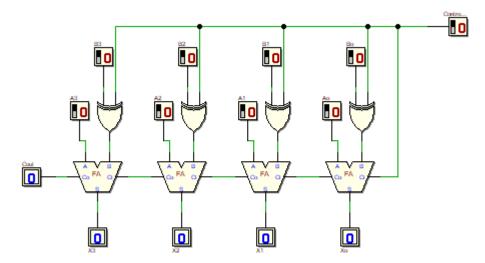


Figure 01: 4-bit adder/subtractor

Code:

```
wire [3:0] B complement; // Complement of B for subtraction
  wire Carry;
                    // Carry output
  // Generate 2's complement of B if SUB is 1
  assign B complement = B ^ {4{SUB}};
  // Perform addition
  assign {CarryOut, Result} = A + B_complement + SUB;
endmodule
`timescale 1ns / 1ps
module testbench;
  reg [3:0] A, B; // 4-bit inputs
                // Subtraction control
  reg SUB;
  wire [3:0] Result; // 4-bit result
  wire CarryOut;
                    // Carry out
  // Instantiate the module under test (adder subtractor)
  adder subtractor uut (
    A(A)
    .CarryOut(CarryOut)
  initial begin
    // Monitor the outputs
    $monitor("Time=%0t | A=%b B=%b SUB=%b => Result=%b CarryOut=%b", $time, A,
B, SUB, Result, CarryOut);
    // Test Cases
    A = 4'b0101; B = 4'b0011; SUB = 0; #10; // Add
    A = 4'b0101; B = 4'b0011; SUB = 1; #10; // Subtract
    A = 4'b1111; B = 4'b0001; SUB = 0; #10; // Add with carry
    A = 4'b1000; B = 4'b1000; SUB = 1; #10; // Subtract with borrow
    A = 4'b0000; B = 4'b0001; SUB = 1; #10; // Edge case: 0 - 1
  end
endmodule
Output:
Time=0 | A=0101 B=0011 SUB=0 => Result=1000 CarryOut=0
Time=10000 | A=0101 B=0011 SUB=1 => Result=0010 CarryOut=1
Time=20000 | A=1111 B=0001 SUB=0 => Result=0000 CarryOut=1
```

Time=30000 | A=1000 B=1000 SUB=1 => Result=0000 CarryOut=1 Time=40000 | A=0000 B=0001 SUB=1 => Result=1111 CarryOut=0

Discussion:

The 4-bit Adder-Subtractor module performs both addition and subtraction based on a control input SUB. When SUB is 0, it adds the inputs A and B; when SUB is 1, it subtracts B from A by inverting B and adding 1 (two's complement). The result is a 4-bit output Result, and a CarryOut signal is generated for overflow detection. This design allows for efficient arithmetic operations in digital systems.